

ECE 100 Assignment 1

1.26) 30 days = 30 * 24 = 720 hours.

$$\frac{\pm 60}{720 \text{ hr}} \cdot \frac{1 \text{ kWh}}{\pm 0.12} \approx 0.6944 \text{ kW} = \boxed{694.4 \text{ W}}$$

$$I = \frac{P}{V} = \frac{694.4 \text{ W}}{120 \text{ V}} = \boxed{5.787 \text{ A}}$$

$$694.4 \text{ W} \rightarrow 60 \text{ W decrease is a } \frac{60}{694.4} = \boxed{8.64 \%} \text{ decrease}$$

1.55) $P = I^2 R = V^2 / R \rightarrow R = V^2 / P = 100^2 / 100 = \boxed{100 \Omega}$


When V is reduced by 10% $\Leftrightarrow V' = \frac{9}{10} V$, $P' = \frac{81}{100} P \Rightarrow \boxed{19 \%}$ reduction

1.61) $P_{\text{voltage source}} = 10 \cdot (-2) = -20 \text{ W}$

$P_{\text{current}} = 10 \cdot (+2) = +20 \text{ W}$ voltage source absorbing power \therefore ok

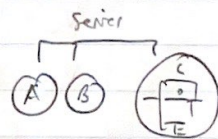1.37) Since $i_b = 2 \text{ A}$, $\boxed{i_a = -2 \text{ A}}$ Since $i_b = 2 \text{ A}$ and it splits into $-i_c$ and 3 A ,

$$\boxed{i_c = 1 \text{ A}} \quad i_c = 1 \text{ A so } \boxed{i_d = 3 + 1 = 4 \text{ A}}$$



A, B are in series, and those are in series with the parallel block (C, D, E)

1.38)

$$i_a = 2 \text{ A}$$

$$i_b = 3 \text{ A}$$

$$i_c = 1 \text{ A}$$

$$i_d = -5 \text{ A}$$

$$i_e = +5 \text{ A}$$

$$i_f = -3 \text{ A}$$

$$i_g = -7 \text{ A}$$

$$i_h = 4 \text{ A}$$

\leftarrow because $a+c=b$

$\leftarrow e+g=b+d$

$\leftarrow d+a=f$

$\leftarrow g+f=h$

$$i_f = i_g + i_h$$

$$i_a + i_c = i_e$$

$$i_b + i_d = i_c + i_e$$

$$i_f + i_c = i_b + i_d$$


$$i_f = 3 - 5 - 1$$

$$\rightarrow i_a + i_c + i_g = i_b + i_d$$

$$i_f + i_c = i_b + i_d$$

$$i_f = 3 - 5 - 1$$

1.43)

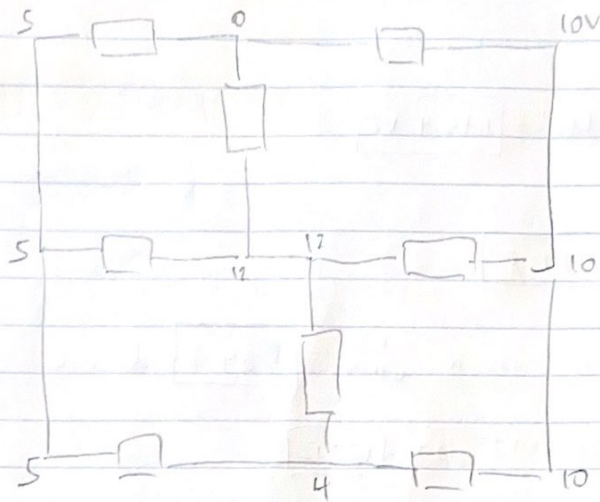

assuming ground, we follow paths to get the final diagram

now, we can find

$$V_d = 12 - 0 = 12V$$

$$V_c = 4 - 5 = -1V$$

$$V_e = 12 - 4 = 8V$$

$$V_g = 12 - 10 = 2V$$

1.44)

A: $V = 10V$ $I = 2A$

$P = 20W$

D: $V = 4V$ $I = -1A$

$P = -4W$

C: $V = 4 - 0 = 4V$ $I = 2 - 1 = 1A$

$P = -4W$

B: $V = 4 - 10 = -6V$ $I = -(-2) = 2A$

$P = -12W$


$0W$

$$I_b = -2A \quad V_c = 4V$$

$$I_c = 1A$$

$$V_b = -6V$$

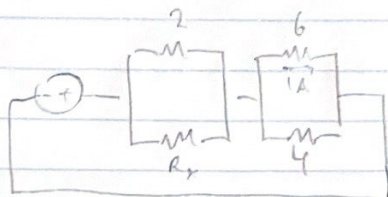1.67) a) the circuit essentially looks like this



the $2/R_x$ pair and the $6/4$ pair and the battery are series.

b) the 2 & R_x are parallel
so is 6 and 4 ohm resistors.

c) $6 \cdot 1A = 6V$ so $\frac{6V}{4\Omega} = 1.5A$ so total I through circuit =

$$1.5 + 1 = 2.5A$$

$10V - 6V = 4V$ across 1st parallel. $\frac{4V}{2\Omega} = 2A$ so other branch

$$\text{has } 2.5A - 2A = 0.5A$$

$$\frac{4}{R_x} = 0.5 \text{ so } R_x = \boxed{8\Omega}$$

1.70) a) $10 - 3 \cdot i_x - 5V_x = 0$

$$b) 10 - 3i_x - 5(3i_x) = 0$$

$$\boxed{V_x = 3i_x = 1.67V}$$

$$i_x = \frac{10}{18} = \frac{5}{9}A$$

$$= \boxed{0.56A}$$

$$c) P_{vs} = -10 \cdot 0.56 = \boxed{-5.6W}$$

$$P_{vs} + P_R + P_{dvs} = 0 \checkmark$$

$$P_R = i^2 R = 0.56^2 \cdot 3 = \boxed{+0.9259W}$$

$$P_{dvs} = 0.56 \cdot 1.67V \cdot 5 = \boxed{+4.6296W}$$

1.75)

$$V_s - 3 \cdot I - 4 \cdot I - 2 \cdot I = 0$$

$$I = \frac{V_s}{2} + 1$$

$$\frac{V_x}{4} = 1$$

$$V_x = 4$$

$$I = 3$$

$$V_s = 9 + 4 + 2 = \boxed{15V}$$