
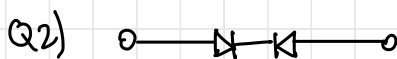


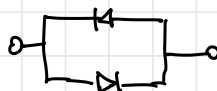$V_D = 0.6 + 5.6 = 6.2V$   
 $-V_D = -6.2V$   
 until current flows



open circuit aka  $\rightarrow \circ$   
 b/c both diodes cannot be alive  
 at the same time.



short circuit aka  $\circ - \circ$   
 b/c both diodes will have exactly 1  
 on so it will short while the other  
 opens.

Q3) if the diodes are all on:

a)  $I = \frac{10V}{2.7k\Omega} = 3.703 \text{ mA}$ ,  $V = 0V$

b)  $I = 0A$ ,  $V = 10V$

c) if diode is on, all current branches into  
 the diode, so  $I = 0$ .  $V_D = 0$  b/c the  
 $V_+ = 0$  and  $V_- = 0$  since  $i = \frac{10}{2.7k} = 3.7mA$

d)  $I_D = 10mA \cdot \frac{1}{1+1} = 5mA$   
 $I = 10mA - I_D = 5mA \rightarrow V = 5 \cdot 1 = 5V$

Q4) assume  $D_1$  on  $D_2$  off  $\rightarrow V = 15 \cdot \frac{10}{10+5}$



a)  $= 10V$ . nothing goes through  $D_2$  so

$I = 0A$   $i_{D1} > 0$   $V_{D2} < 0$  b/c

$V_{D2} = 15 \cdot \frac{5}{10+5} - 10 = -5 \checkmark$

b) assume  $D_1$  on  $D_2$  off:  $I = \frac{6}{1k} = 6mA$   
 $V_{D_2} = 3 - 6 = -3V < 0$ ,  $I_{D_1} > 0$  ✓  
 $V = 6V$ ,  $I = 6mA$

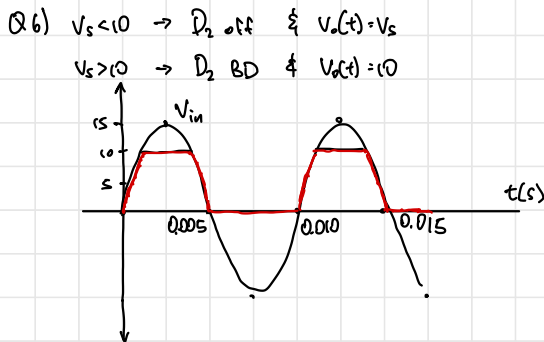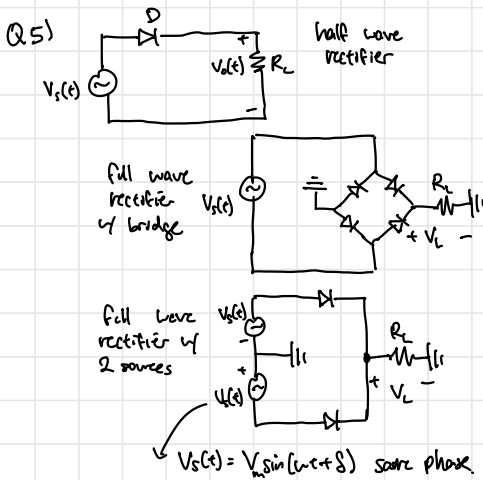c) assume  $D_1$  on  $D_2$  on:  
 $I_{D_1} = 15V/1k + 30V/2.2k$   
 $= 15mA + 13.636mA = 28.636mA > 0$   
 $I_{D_2} = 13.636mA + 30/1.5k = 33.636mA > 0$  ✓  
 $I = 33.64mA$ ,  $V = 30V$ .



Q7)  $I_O = I_S \cdot e^{V_D/(nV_T)} - 1 \rightarrow I_S = \frac{I_O}{e^{V_D/(nV_T)} - 1} = \frac{0.2mA}{e^{0.6V/(2 \cdot 26mV)} - 1}$   
 $I_S = 1.95nA$   
 $V_{D_2} = 0.65V \rightarrow i_{D_1} = 1.95nA \cdot e^{0.65V/(2 \cdot 26mV)} = 0.523mA$   
 $V_{D_3} = 0.7V \rightarrow i_{D_2} = 1.95nA \cdot e^{0.7V/(2 \cdot 26mV)} = 1.364mA$

Q8)  $-V_s + i_x R_S + V_x = 0 \Rightarrow i_x = \frac{V_s - V_x}{R_S} = \frac{3V - V_x}{1} = 3 - V_x$

Point 1:  $V_x = V_s = 3$ ,  $i_x = 0 \rightarrow (3, 0)$

2:  $V_x = 0$ ,  $i_x = \frac{V_s}{R_S} = 3 \rightarrow (0, 3)$

$-V_x + 3 = (e^{V_x} - 1)/10$

graphing calc  $\rightarrow V_x = 2.194$ ,  $i_x = 801mA$

Q9)  $V_s(t) = 5 \sin(200\pi t) - 5$



Q10)  $D_1$  on  $D_2$  off with  $V_{in} < 0 \rightarrow V_{C1} = -V_m$   
 $D_1$  off  $D_2$  on with  $V_{in} > 0 \rightarrow V_{C2} = V_s - V_{C1}$   
 $V_C = V_{C2} = V_s - V_{C1} = 2V_m \rightarrow$  voltage doubler

