 


Due **Tuesday, February 22<sup>nd</sup> 2022, by 6 pm** to Gradescope.  
100 points total.


### Diode – Lecture 11

Q1 (10 points)

Sketch  $i$  versus  $v$  to scale for the circuits show below. The reverse-breakdown voltages of the Zener diodes are shown. Assume voltages of 0.6 V for all diodes including the Zener diodes when current flows in the forward direction.



S1

 

Q2 (10 points)

Two ideal diodes are placed in series, pointing in opposite directions. What is the equivalent circuit for the combination? What is the equivalent circuit if the diodes are in parallel and pointing in opposite directions?


S2

The equivalent circuit for two ideal diodes in series pointing in opposite directions is an open circuit because current cannot flow in the reverse direction for either diode.

The equivalent circuit for two ideal diodes in parallel pointing in opposite directions is a short circuit because one of the diodes is forward conducting for either direction of current flow.

 Q3 (10 points)

Find the values of  $I$  and  $V$  for the circuits of Figure below, assuming that the diodes are ideal.




S3

- (a) The diode is on,  $V = 0$  and  $I = \frac{10}{2700} = 3.70\text{ mA}$ .
- (b) The diode is off,  $I = 0$  and  $V = 10\text{ V}$ .
- (c) The diode is on,  $V = 0$  and  $I = 0$ .
- (d) The diode is on,  $I = 5\text{ mA}$  and  $V = 5\text{ V}$ .

 Q4 (10 points)

Find the values of  $I$  and  $V$  for the circuits of Figure below, assuming that the diodes are ideal.



S4


- (a)  $D_1$  is on and  $D_2$  is off.  $V = 10$  volts and  $I = 0$ .
- (b)  $D_1$  is on and  $D_2$  is off.  $V = 6$  volts and  $I = 6\text{ mA}$ .
- (c) Both  $D_1$  and  $D_2$  are on.  $V = 30$  volts and  $I = 33.6\text{ mA}$ .

Q5 (10 points)


**P9.49.** Draw the circuit diagram of a half-wave rectifier for producing a nearly steady dc voltage from an ac source. Draw two different full-wave circuits.

S5

 Half-wave rectifier with a capacitance to smooth the output voltage:




Full-wave circuits:

 

 
Q6 (10 points)

**P9.63.** Sketch to scale the output waveform for the circuit shown in Figure P9.63. Assume that the diodes are ideal.



S6

 Refer to Figure P9.63 in the book. When the source voltage is negative, diode  $D_3$  is on and the output  $v_o(t)$  is zero. For source voltages between 0 and 10 V, none of the diodes conducts and  $v_o(t) = v_s(t)$ . Finally when the source voltage exceeds 10 V,  $D_1$  is on and  $D_2$  is in the breakdown region so the output voltage is 10 V. The waveform is:



## Diode – Lecture 12

Q7 (10 points)

We have a junction diode that has  $i_D = 0.2$  mA for  $v_D = 0.6$  V. Assume that  $n=2$  and  $V_T = 0.026$  V. Use the Shockley equation to compute the diode current at  $v_D = 0.65$  V and at  $v_D = 0.70$  V.

S7

For  $v_D = 0.6$  V, we have

$$i_D = 0.2 \times 10^{-3} = I_s \left[ \exp(v_D/nV_T) - 1 \right] \\ \cong I_s \exp(v_D/nV_T)$$

Thus, we determine that:

$$I_s \cong \frac{i_D}{\exp(v_D/nV_T)} = \frac{0.2 \times 10^{-3}}{\exp(0.6/(2 \times 0.026))} = 1.950 \times 10^{-9} \text{ A}$$

Then, for  $v_D = 0.65$  V, we have

$$i_D \cong I_s [\exp(0.650/0.052) - 1] = 0.5321 \text{ mA}$$

Similarly, for  $v_D = 0.700$  V, we find  $i_D = 1.369$  mA.


Q8 (10 points)

$v_x$  and  $i_x$

techniques to solve for  $v_x$  and  $i_x$ .

$$i_x = [\exp(v_x) - 1]/10$$

Ω. Use graphical load-line

 

S8

The load-line equation is

$$V_s = R_s i_x + v_x$$


Substituting values, this becomes

$$3 = i_x + v_x$$

Next, we plot the nonlinear device characteristic equation


$$i_x = [\exp(v_x) - 1]/10$$

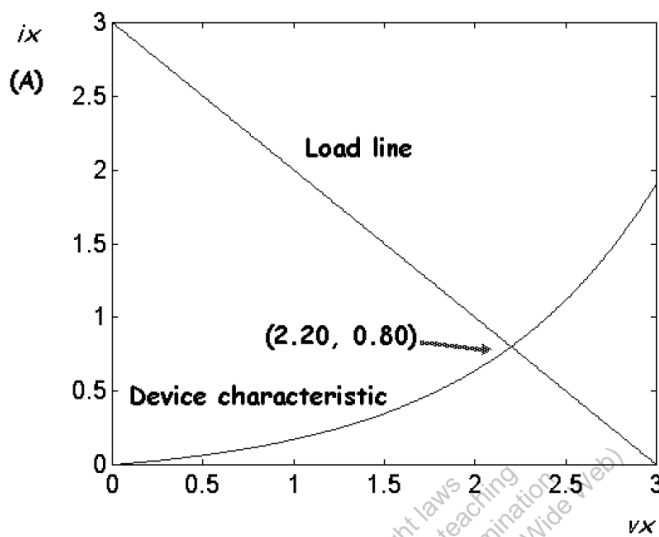and the load line on the same set of axes. Finally, the solution is at the intersection of the load line and the characteristic as shown:




Q9 (10 points)

**P9.71. Voltage-doubler circuit.** Consider the circuit of **Figure P9.71**. The capacitors are very large, so they discharge only a very small amount per cycle. (Thus, no ac voltage appears across the capacitors, and the ac input plus the dc voltage of  $C_1$  must appear at point A.) Sketch the voltage at point A versus time. Find the voltage across the load. Why is this called a voltage doubler? What is the PIV across each diode?

 

**Figure P9.71**

S9

 


The capacitor  $C_1$  and diode  $D_1$  act as a clamp circuit that clamps the negative peak of  $v_A(t)$  to zero. Thus, the waveform at point A is:



Diode  $D_2$  and capacitor  $C_2$  act as a half-wave peak rectifier. Thus, the voltage across  $R_L$  is the peak value of  $v_A(t)$ . Thus,  $v_L(t) \cong 2V_m$ . This is called a voltage-doubler circuit because the load voltage is twice the peak value of the ac input. The peak inverse voltage is  $2V_m$  for both diodes.

Q10 (10 points)


**P9.69.** Consider the circuit shown in **Figure P9.69**, in which the  $RC$  time constant is very long compared with the period of the input and in which the diode is ideal. Sketch  $v_o(t)$  to scale versus time.

 

**Figure P9.69**


S10

 This is a clamp circuit that clamps the positive peaks to zero.



Due **Tuesday, March 8<sup>th</sup> 2022, by 9 pm** to Gradescope.  
100 points total.

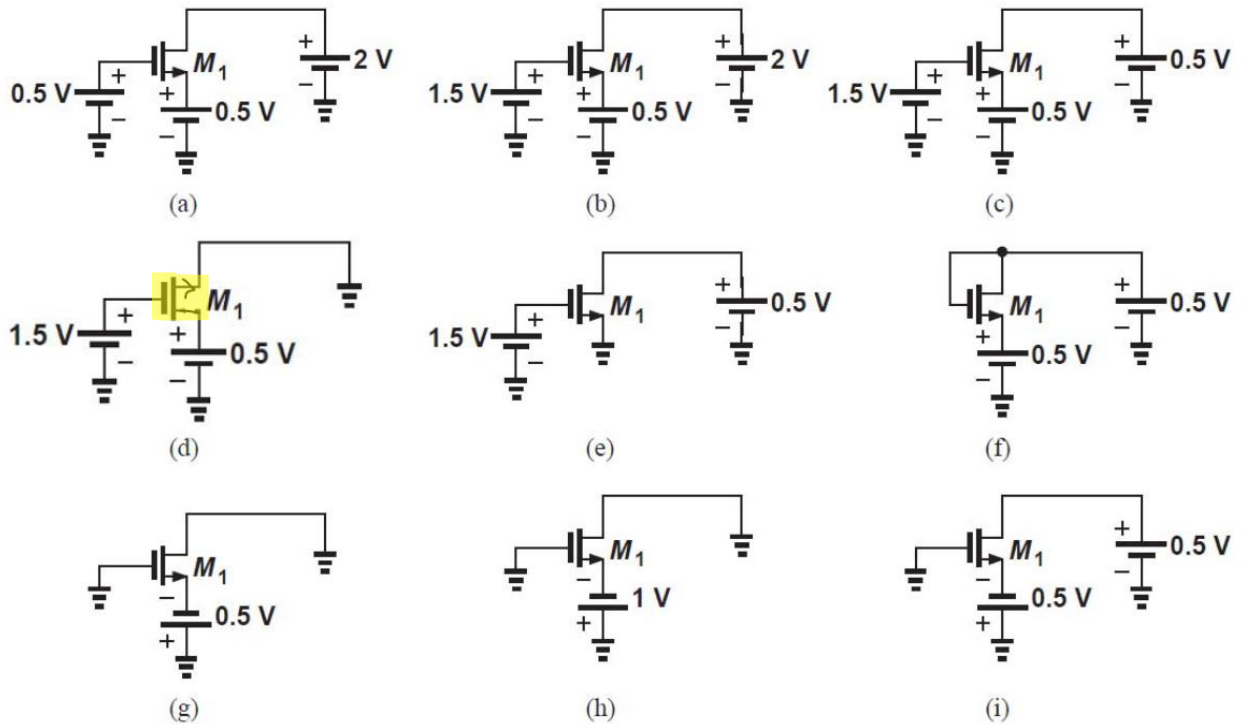Q1. (36 marks) **MOSFET as a Resistor**: If the **threshold is equal to 0.7 V**, for each circuit determine whether the device is off or



| Circuit | Drain voltage ( $V_D$ ) | Source voltage ( $V_S$ ) | Gate voltage ( $V_G$ ) | State of MOSFET (OFF/Res/Sat) |
|---------|-------------------------|--------------------------|------------------------|-------------------------------|
| A       | 2                       | 0.5                      | 0.5                    | Off                           |
| B       | 2                       | 0.5                      | 1.5                    | Sat                           |
| C       | 0.5                     | 0.5                      | 1.5                    | Res                           |
| D       | 0.5                     | 0                        | 1.5                    | Res                           |
| E       | 0.5                     | 0                        | 1.5                    | Res                           |
| F       | 0.5                     | 0.5                      | 0.5                    | Off                           |
| G       | 0                       | -0.5                     | 0                      | Off                           |
| H       | 0                       | -1                       | 0                      | Sat                           |
| I       | 0.5                     | -0.5                     | 0                      | Off                           |



Q2. (10 points)

In the figure alongside:  $V_{GS} = 5V$ ,  $V_{DD} = 10V$  and  $R_D = 1k\Omega$ ,  $V_{th} = 0.7V$

$K = 0.24E-3 \text{ A/V}^2$

Draw the small-signal model for the MOSFET and report

- Transconductance
- Output resistance
- Gain
- Identify the mode operation of the transistor. (CS/CD etc)


(Hint : Refer to Lecture slides)

$$I_d = k (V_{GS} - V_{th})^2 = 0.24E-3 \times (5 - 0.7)^2 = 4.4376E-3 \text{ Amp}$$



$$G_m = 2k(V_{GS} - V_{th}) = 2.064E-3 \text{ /ohm}$$

$$\text{Output resistance} = R_D = 1K\Omega$$

 
$$\text{Gain} = -g_m \times R_D = -2.064$$



## MOSFET Common-Source Amplifier

  

 Source terminal is shared by input and output




$$v_{gs} = v_{in} \quad v_o = -g_m v_{in} R_D$$

$$\text{Gain: } A_v = \frac{v_o}{v_{in}} = -g_m R_D$$

$$\text{Input Impedance: } R_{in} = \infty$$
 
$$\text{Output Impedance: } R_{out} = R_D$$




Q3. (10 points)

Determine  $I_{DQ}$ ,  $V_{DSQ}$ ,  $V_{GSQ}$  for this MOSFET.

 **(Hint: Find Q point and assume transistor is in Saturation)**

( $k = 0.24 \text{E-}3 \text{ A/V}^2$ )

**$V_{th} = 3\text{V}$** ,  $V_{DD} = 12\text{V}$ ,  $R_D = 2\text{k}\Omega$



Solution :

Here, current through 10Mohm is assumed to be zero, since the input gate current of a MOSFET is very negligible.

Therefore,  $V_{GS} \approx V_{DS}$  and the entire drain current from battery will flow into the MOSFET.

Now its given that the transistor is in the saturation.

Hence,  $I_d = k(V_{GS} - V_{th})^2 = 0.24\text{E-}3 \times (V_{GS} - 3)^2$

Now, using KCL at the drain of the transistor,

$I_d = (12 - V_{DS}) / 2\text{k}$

Since  $V_{GS} \approx V_{DS}$ , equating the above two equations, we get :

$0.24\text{E-}3 \times (V_{GS} - 3)^2 = (12 - V_{GS}) / 2\text{k} \rightarrow$  Solving for VGS gives  **$V_{GS} = V_{DS} = 6.411\text{V} = V_{GSQ} = V_{DSQ}$**

**$I_d = 0.24\text{E-}3 (6.411 - 3)^2 = 2.79\text{mA}$**

Q4. (15 points)

Determine  $I_{DQ}$ ,  $V_{GSQ}$ , and  $V_{DSQ}$ .

**$V_{th} = 5\text{V}$** ,  $K = 0.12\text{E-}3 \text{ A/V}^2$

**(Hint: Find Q point and assume transistor is in Saturation)**

**Solution:**

By voltage divider:  $V_G = 40 \times 18 / (18 + 22) = 18\text{V}$

By KVL at input :  $V_{GS} = V_G - I_D \times R_S$

Thus,  $I_D = (V_G - V_{GS}) / R_S = (18 - V_{GS}) / 0.82\text{k}$


Given that transistor is in saturation:

$I_D = k (V_{GS} - V_{th})^2 = 0.12\text{E-}3 (V_{GS} - 5)^2$

Equating the above two equations of  $I_D$  and solving for  $V_{GS}$ , we get:


**$V_{GS} = 12.485\text{V}$** , and hence  **$I_D = 6.723\text{mA}$**  and  $V_{DS} = V_{DD} - I_D (R_D + R_S)$

 Therefore  $V_{DS} = 40 - 6.723\text{E-}3 (3000 + 820) = \textbf{14.31V}$




 Q5. (15 points)


Consider :  $Y = (A + B) \cdot C$  where A, B, C are digital inputs [Read this as,  $Y = (A \text{ OR } B) \text{ AND } C$  ]. Implement Y by taking inputs as A, B, C and using NMOS and/or PMOS. You are allowed to use a resistor as well.



PMOS

 


# PMOS + NMOS

 

Q6. (14 points)


For the circuit shown below, fill in the Truth Table below with 'D' as output and X, Y, Z as input for all possible input combinations. Also, write the Boolean expression for D in terms of X, Y, Z.

| Z | Y | X | D |
|---|---|---|---|
|   |   |   |   |
|   |   |   |   |
|   |   |   |   |
|   |   |   |   |
|   |   |   |   |
|   |   |   |   |
|   |   |   |   |
|   |   |   |   |

 


| Z | Y | X | D |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

(a)

 

(b)

 

(c)

$$D = \overline{(X + Y) \cdot Z}$$


(d)

Due **Thursday, March 10<sup>th</sup> 2022, by 6 pm** to Gradescope.  
100 points total.

### Operational Amplifier – Lecture 15, 16

 
Q1 (20 points)

Sketch  $v_{in}(t)$  and  $v_o(t)$  to scale versus time for the circuit shown in Figure. The op amp is ideal.




S1

 This is an inverting amplifier having a voltage gain given by  $A_v = -R_2/R_1 = -3$ . Thus, we have  $v_o(t) = -3 \times [2 \cos(2000\pi t)]$ . Sketches of  $v_{in}(t)$  and  $v_o(t)$  are



 
Q2 (20 points)

For each of the circuits shown in Figure, assume that the op amp is ideal and find the value of  $v_o$ . The circuit has negative feedback, and the summing-point constraint (virtual open-circuit principle) applies.




S2
 
$$v_o = -(1\text{ k}\Omega) \times 2\text{ mA} = -2\text{ V}$$




Q3 (20 points)

 

S3



 Because of the summing-point constraint, the voltages across the two resistors of value  $R$  are equal. Thus, the currents in the resistors of value  $R$  are equal as indicated:




Then applying KVL, we have  $v_{in} = 2R(2i) + Ri$  and  $v_o = -15Ri$ . Solving, we find  $A_v = \frac{v_o}{v_{in}} = -3$ .

 Q4 (20 points)

The op amp shown below is ideal, except that the extreme output voltages that it can produce are  $\pm 10$  V. Determine two possible values for each of the voltages shown.

[Hint: Notice that this circuit has positive feedback so the summing-point constraint does not apply.]



S4

This circuit has positive feedback and the output can be either +10 V or -10 V. Writing a current equation at the inverting input terminal of the op amp we have

$$\frac{v_x - 2}{1000} + \frac{v_x - v_o}{2000} = 0$$

Solving we find

$$v_x = 1.3333 + 0.3333v_o$$

For  $v_o = 10$  V, we have  $v_x = 4.667$  V. On the other hand for  $v_o = -10$  V, we have  $v_x = -2$  V. Notice that for  $v_x$  positive the output remains stuck at its positive extreme and for  $v_x$  negative the output remains stuck at its negative extreme.

Q5 (20 points)

**P13.33.** Derive an expression for the voltage gain of the circuit shown in **Figure P13.33** as a function of  $T$ , assuming an ideal op amp. ( $T$  varies from 0 to unity, depending on the position of the wiper of the potentiometer.)


 


Figure P13.33

S5

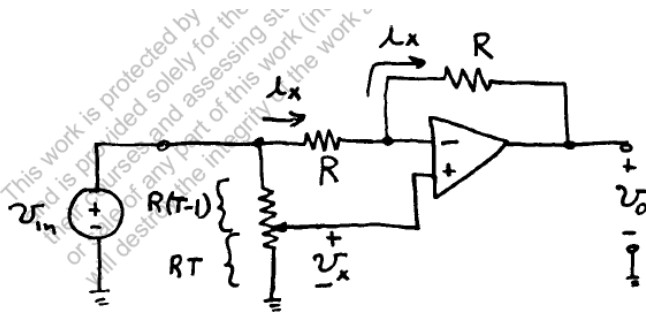

By the voltage-division principle, we have

$$v_x = \frac{RT}{RT + (1-T)R} v_{in} = T v_{in}$$

Then, we can write

$$i_x = \frac{v_{in} - v_x}{R} = \frac{v_{in}(1-T)}{R}$$

$$\begin{aligned} v_o &= -R i_x + v_x \\ &= -v_{in}(1-T) + T v_{in} \\ &= v_{in}(2T-1) \end{aligned}$$

Thus, as  $T$  varies from 0 to unity, the circuit gain varies from -1 through to 0 to +1.